

1) Calculate for the following circuit:

- a. Total capacitance
- b. Total charge and charge on each capacitor

